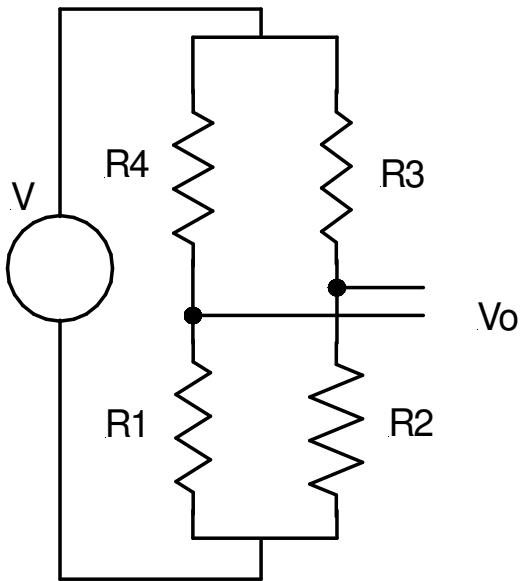


PUENTES DE MEDIDA



$$V_o = \left(\frac{R2}{R2 + R3} - \frac{R1}{R1 + R4} \right) V =$$

$$= \frac{\frac{R4}{R1} - \frac{R3}{R2}}{\left(1 + \frac{R4}{R1}\right) \left(1 + \frac{R3}{R2}\right)} V$$

Si $\frac{R4}{R1} = \frac{R3}{R2}$ $V_o = 0$

Si $R1 = R2 = R4 = R$ (un solo elemento variable)
y $R3 = R(1 + \delta)$

$$V_o = \frac{\delta V}{2(2 + \delta)}$$


Si $R2 = R4 = R$
y $R1 = R3 = R(1 + \delta)$ (mayor sensibilidad)

$$V_o = \frac{1 - (1 + \delta)^2}{(2 + \delta)^2} V \cong \frac{2\delta}{\delta + 1} V$$

Si $R1 = R4 = R$
y $R2 = R(1 + \delta)$
 $R3 = R(1 - \delta)$


$$V_o = \frac{\delta}{2} V$$

LINEALIZACIÓN

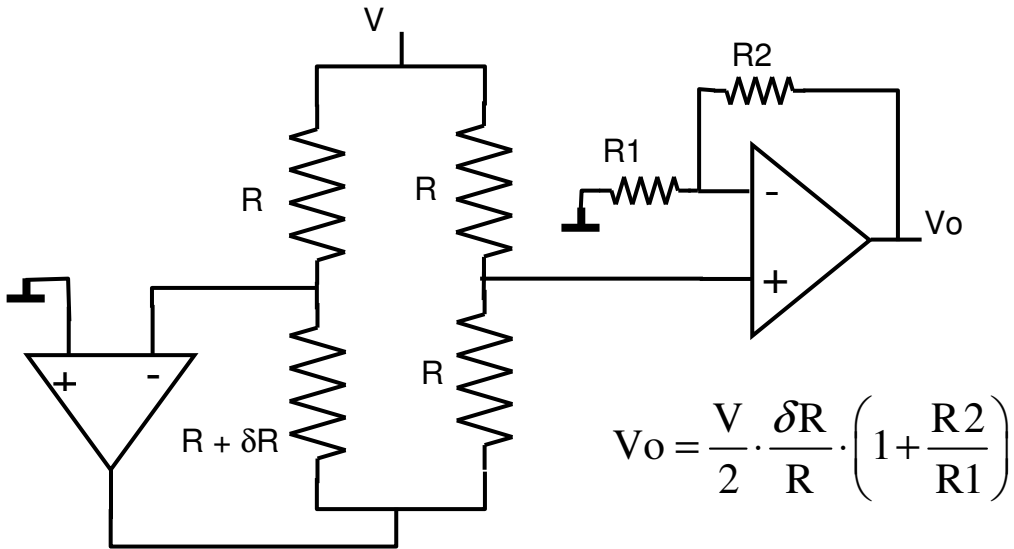




$$V_o = \frac{V}{2} \cdot \frac{\delta R}{R} \cdot \left(1 + \frac{R2}{R1} \right)$$

AUTOBALANCE

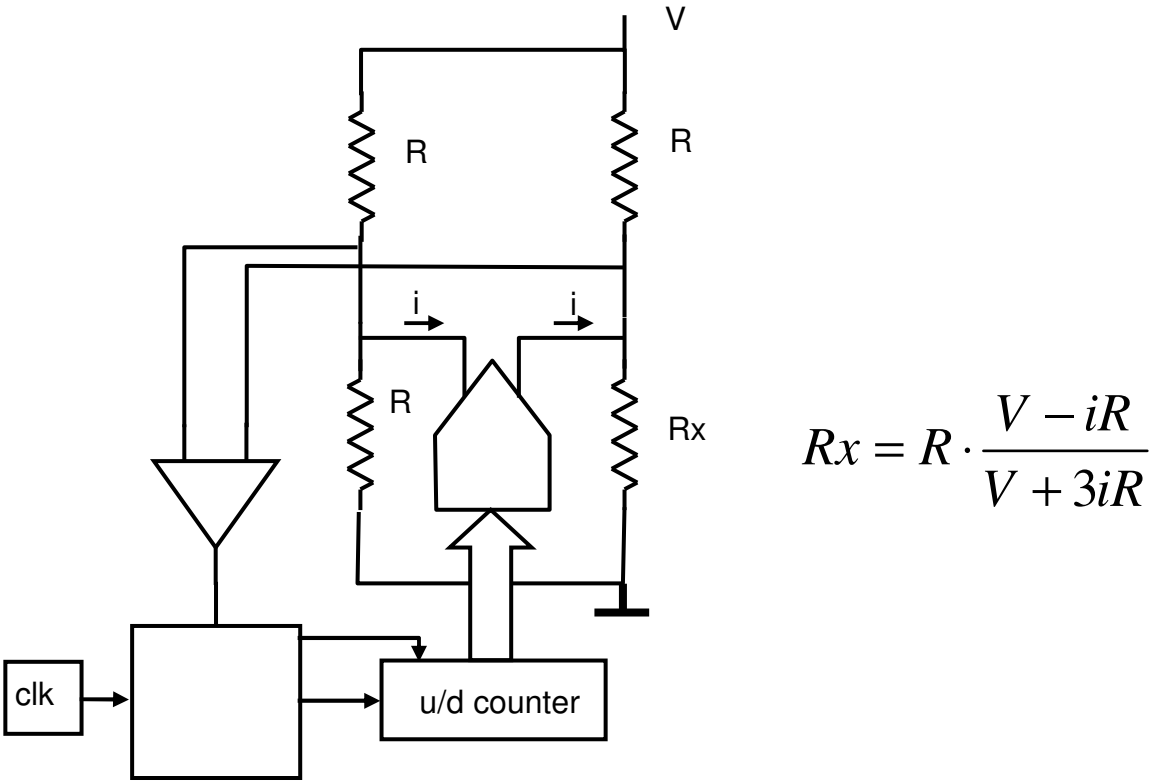


$$R_x = R \cdot \frac{V - iR}{V + 3iR}$$

CONFIGURACIONES

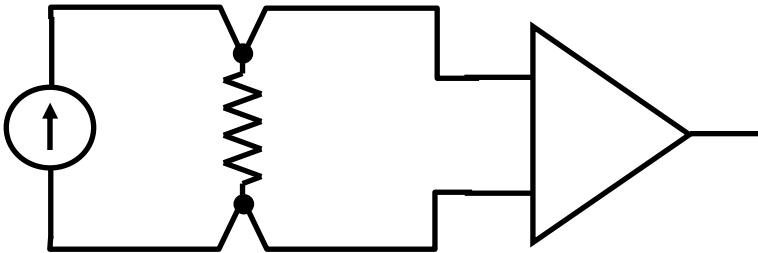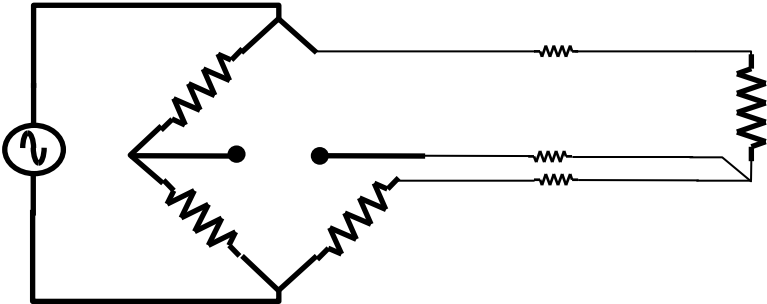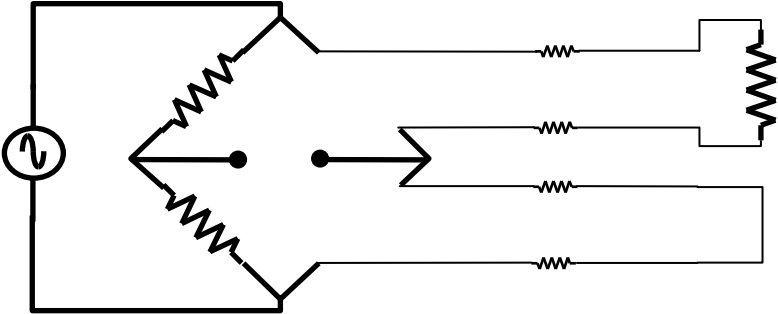

PUENTES DE IMPEDANCIA:


OWEN

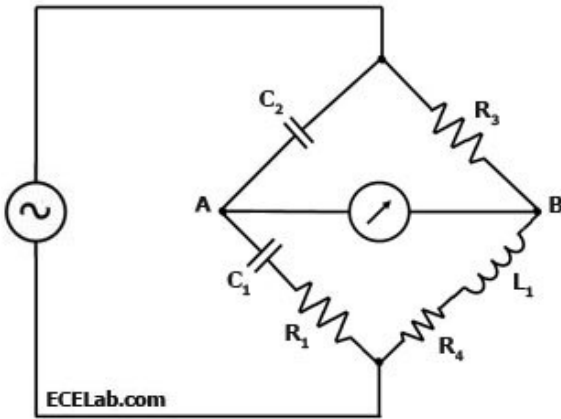

$$L_1 = C_2 \cdot R_3 \cdot R_1$$

$$R_4 = \frac{C_2 \cdot R_3}{C_1}$$

SCHERING

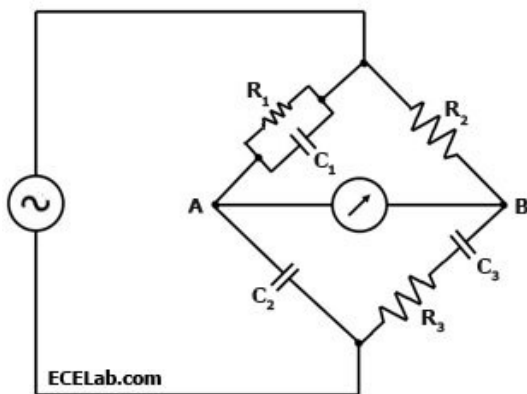


$$R_3 = \frac{C_1 \cdot R_2}{C_2}$$

$$C_3 = \frac{R_1 \cdot C_2}{R_2}$$

$$D = \omega \cdot C_1 \cdot R_1$$

WIEN

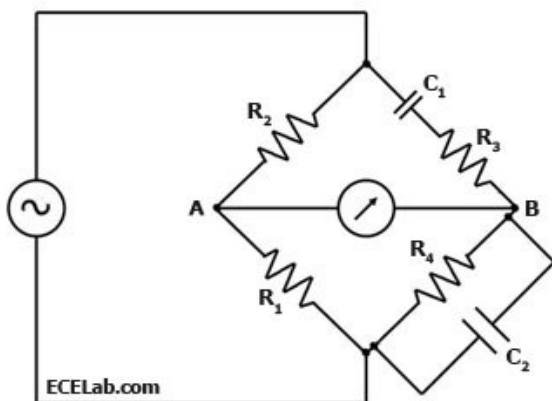

$$f = \frac{1}{2\pi} \cdot \sqrt{\frac{1}{R_3 \cdot R_4 \cdot C_1 \cdot C_2}}$$